

Lab Report #1(Resubmit)

Name: Ruochen Duan

Student ID: 1405106

The modified parts are SignExtend and LeftShift2, and the entity name of MUX32 is changed to MUX64.

Explanation and Description

① AND2

I choose the behavioral for modeling type. And the truth table of the AND2 gate is

In0	In1	Output
0	0	0
0	1	0
1	0	0
1	1	1

My testbench is that during the simulation of 200ns, I first set

In0 = 0 In1 = 0 for 50ns

Then set

In0 = 0 In1 = 1 for 50ns

Then set

In0 = 1 In1 = 0 for 50ns

Then set

In0 = 1 In1 = 1

The result is showed in Figure 1

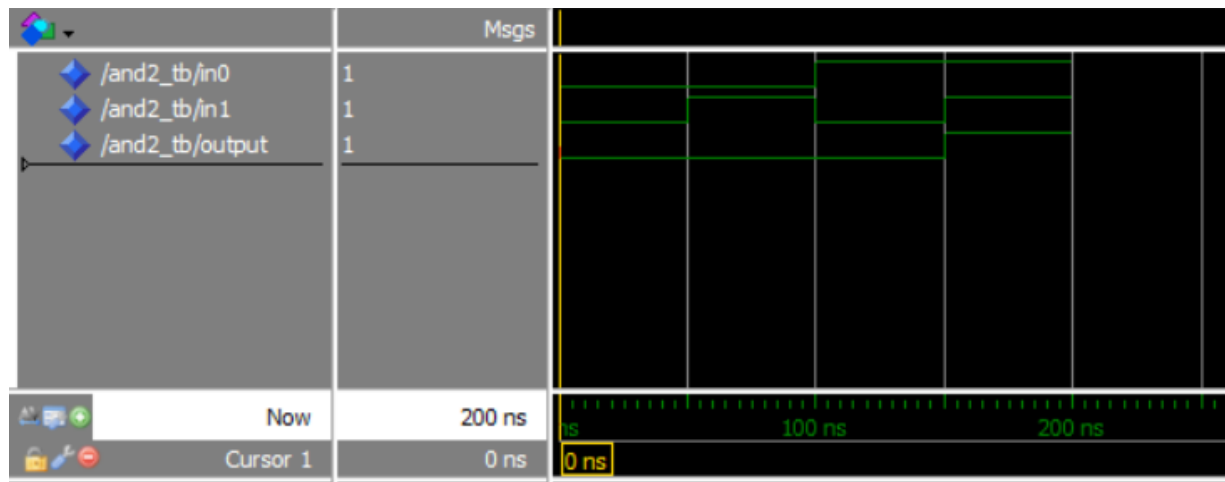


Figure 1

We can see from the Figure 1 that the output is '1' during $t = 150 \text{ ns}$ to $t = 200 \text{ ns}$. The simulation results are the same as the truth table.

② MUX5

I choose the behavioral for modeling type. MUX5 is a two by one mux with 5-bit inputs/outputs. When the $\text{sel} = 0$, the output = in0. When the $\text{sel} = 1$, the output = in1.

My testbench is that during the simulation of 200ns, I first set

$\text{Sel} = 1$ $\text{In0} = \text{"00000"}$ $\text{In1} = \text{"11110"}$ for 50 ns

Then set

$\text{Sel} = 1$ $\text{In0} = \text{"00000"}$ $\text{In1} = \text{"10100"}$ for 50 ns

Then set

$\text{Sel} = 0$ $\text{In0} = \text{"01100"}$ $\text{In1} = \text{"10100"}$ for 50 ns

Then set

$\text{Sel} = 0$ $\text{In0} = \text{"10010"}$ $\text{In1} = \text{"01010"}$

The simulation result is showed in Figure 2

 


Figure 4(t=100ns to t=200ns)

We can see from the simulation result that
 during $t = 0 \text{ ns}$ to $t = 50 \text{ ns}$,
 the output is equal to the input of In1, when $\text{sel} = 1$.
 during $t = 50 \text{ ns}$ to $t = 100 \text{ ns}$,
 the output is equal to the input of In1, when $\text{sel} = 1$.
 during $t = 100 \text{ ns}$ to $t = 150 \text{ ns}$,
 the output is equal to the input of In0, when $\text{sel} = 0$.
 during $t = 150 \text{ ns}$ to $t = 200 \text{ ns}$,
 the output is equal to the input of In0, when $\text{sel} = 0$. Even the input of In1 is changed.

④ SignExtend(code and testbench are modified)

Before

```

architecture behv1 of SignExtend is
begin
  y <= "00000000000000000000000000000000"& x(31 downto 0);
end behv1;

```

After

```

architecture behv1 of SignExtend is
begin
  process(x)
  begin
    if (x(31)='1') then
      y<=x"ffffffff"&x;
    else
      y<=x"00000000"&x;
    end if;
  end process;
end behv1;

```

I choose the behavioral for modeling type. The function of SignExtend is to extend a 32-bit input to a 64-bit output by extending the most significant bit.

My testbench is that during the simulation of 200ns, I first set

x = x"11110000" for 50 ns

then set

x = x"01010101" for 50 ns

the set

x = x "f0001111" for 50 ns (modified)

the set

x = x "10110100"

The simulation result is showed in Figure 5 and Figure 6

 


Figure 5(t=0ns to t=100ns)

 


Figure 6(t=100ns to t=200ns)

We can see from the simulation result that the value of the output y is same as the input x, but the length of the signal is changed.

⑤ Shift Left 2(code is modified)

Before

```
architecture behv1 of ShiftLeft2 is
begin
    y(63 downto 2) <= x(61 downto 0);
end behv1;
```

After

```
architecture behv1 of ShiftLeft2 is
begin
    y(63 downto 0) <= x(61 downto 0) & "00";
end behv1;
```

I choose the behavioral for modeling type. The function of ShiftLeft2 is to Shifts the input by 2 bits. The input bits higher than 32 will be discarded and 0s will be added on the lowest two bits of the input.

My testbench is that during the simulation of 200ns, I first set

x = x "00000000000000010" for 50 ns

then set

x = x " 0101010101010101" for 50 ns

the set

x = x " FFFFFFFF" for 50 ns

the set

$x = x \ll 1$

The simulation result is showed in Figure 7 and Figure 8

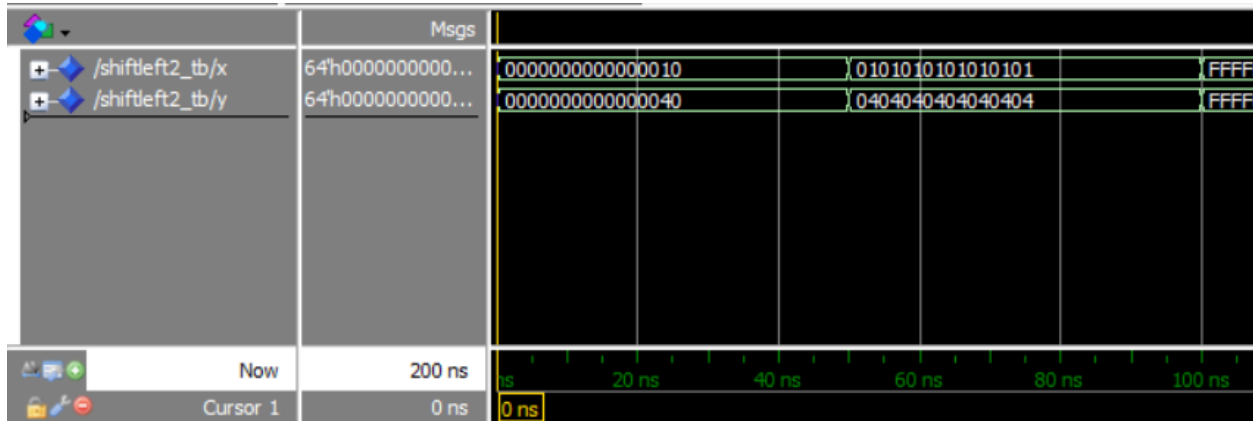


Figure 7(t=0ns to t=100ns)



Figure 8(t=100ns to t=200ns)

We can see from the simulation result that

During the $t = 0 \text{ ns}$ to 50 ns
 $y = x \ll 2$ which is input x shifting 2 bits toward left.

During the $t = 50 \text{ ns}$ to 100 ns
 $y = x \ll 2$ which is input x shifting 2 bits toward left.

During the $t = 100 \text{ ns}$ to 150 ns
 $y = x \ll 2$ which is input x shifting 2 bits toward left.

During the $t = 150 \text{ ns}$ to 200 ns
 $y = x \ll 2$ which is input x shifting 2 bits toward left.

⑥ PC

I choose the behavioral for modeling type. PC is program counter. The PC in the Lab has 4 input which are clk, write_enable, rst and AddressIn and has one output which is AddressOut. The main function of this PC is controlled by the clk and write_enable. When the PC receive the rising-edge of clk(which means the moment clk is changed to '1' form '0') and write_enable ='1' at that time, the input of AddressIn will be assigned to output AddressOut (AddressOut = AddressIn). But at any situation ,when the rst = 1, the output AddressOut will be changed to x"000000000000000000".

My testbench is that during the simulation of 600ns, I first set

```
clk = 0
write_enable=1
rst = 0
AddressIn = x"aaaaaaaaaaaaaaaa" for 50 ns
```

then set

```
clk = 1
write_enable=1
rst = 0
AddressIn keeps its value for 50 ns
```

then set

```
clk = 0
write_enable=1
rst = 1
AddressIn = x"1234123412341234" for 50 ns
```

then set

```
clk = 1
write_enable=1
rst = 1
AddressIn keeps its value for 50 ns
```

then set

```
clk = 0
write_enable=1
rst = 0
AddressIn = x"cccccccccccccccc" for 50 ns
```

then set
clk = 1
write_enable=1
rst = 0
AddressIn keeps its value for 50 ns

then set
clk = 0
write_enable=1
rst = 0
AddressIn = x"4567456745674567" for 50 ns

then set
clk = 0
write_enable=1
rst = 0
AddressIn keeps its value for 50 ns

then set
clk = 0
write_enable=1
rst = 0
AddressIn = x"FFFFFFFFFFFFFFFF" for 50 ns

then set
clk = 1
write_enable=1
rst = 0
AddressIn keeps its value for 50 ns

then set
clk = 1
write_enable=1
rst = 0
AddressIn = x"aaaaaaaaaaaaaaaa" for 50 ns

then set
clk = 0
write_enable=0
rst = 1
AddressIn keeps its value for 50 ns

The simulation result is showed in Figure 9 and Figure 14. And I will analyze the result under each Figure.

 


Figure 9(t=0ns to t=100ns)

We can see from the Figure 9 that

During $t = 0 \text{ ns}$ to $t = 50 \text{ ns}$, the output AddressOut = 0, because rst = '0'.

At $t = 50 \text{ ns}$, the output AddressOut changed its value to x"AAAAAAAAAAAAAAAA", because at that time the PC received a rising edge of clk and write_enable = 1, so the value of AddressIn was assigned to AddressOut.

 


Figure 10(t=100ns to t=200ns)

We can see from the Figure 9 that

At $t = 100 \text{ ns}$, the output AddressOut was changed to 0 from x"AAAAAAAAAAAAAAAA", because at that time the signal rst is set to 1.

At $t = 150 \text{ ns}$, the output AddressOut was still 0 even at that moment the PC received a rising edge of clk and write_enable = 0. Because rst was set to 1 during $t = 100 \text{ ns}$ to $t = 200 \text{ ns}$.

 


Figure 11($t=200\text{ns}$ to $t=300\text{ns}$)

At $t=250\text{ ns}$, the output AddressOut changed its value to x"CCCCCCCCCCCCCCCC", because at that time the PC received a rising edge of clk and write_enable =1, so the value of AddressIn was assigned to AddressOut.

 


Figure 12($t=300\text{ns}$ to $t=400\text{ns}$)

During $t = 300\text{ns}$ to $t = 400\text{ns}$, I set $\text{clk} = 0$. We can see that the value of AddressOut was not changed at time $t = 300\text{ ns}$, even write_enable =1 and AddressIn was changed to x"4567456745674567".

 


Figure 13($t=400\text{ns}$ to $t=500\text{ns}$)

At $t=450$ ns, the output AddressOut changed its value to $x\text{"FFFFFFFFFFFFFFFF"}\text{"}$, because at that time the PC received a rising edge of clk and write_enable = 1, so the value of AddressIn was assigned to AddressOut.

 


Figure 14($t=500\text{ns}$ to $t=600\text{ns}$)

At $t=550$ ns, the output AddressOut didn't change its value to $x\text{"AAAAAAAAAAAAAAAA"}\text{"}$, even write_enable = 1 and rst = 0, because at that time the PC received a falling edge of clk, so the value of AddressIn was not assigned to AddressOut.